

BASIC ELECTRICAL ENGINEERING: COMPREHENSIVE MODULE

1. DC Circuit Analysis: Beyond Ohm's Law

Network Theorems

Thevenin's Theorem Any linear bilateral network can be replaced by an equivalent circuit containing a voltage source (V_{th}) in series with a resistor (R_{th}). This is essential for simplifying complex circuits.

Norton's Theorem Similar to Thevenin, but uses a current source (I_n) in parallel with a resistor (R_n).

Superposition Theorem In a circuit with multiple sources, the current in any branch is the algebraic sum of currents produced by each source acting independently.

2. Single Phase AC Circuits

Complex Impedance &

AC signals are represented as rotating phasors. Impedance (Z) is defined as $R + jX$, where X is reactance.

$$Z = \sqrt{R^2 + X^2} \angle \tan^{-1}(X/R)$$

Power Factor Crucial for efficiency, defined as the cosine of the phase angle between voltage and current. Unity power factor ($\cos\phi=1$) is ideal.

3. Transformers: Principles of Induction

The Ideal Transformer

Transformers work on mutual induction. The transformation ratio (k) determines the voltage step-up or step-down characteristic.

$$k = N_2/N_1 = V_2/V_1 = I_1/I_2$$

Losses: Iron losses (hysteresis and eddy current) and Copper losses (I^2R loss) constitute total power loss.

4. Advanced Problem Bank

Complex Impedance &

AC signals are represented as rotating phasors. Impedance (Z) is defined as $R + jX$, where X reactance

$$Z = \sqrt{R^2 + X^2} \angle \tan^{-1}(X/R)$$

Power Crucial for efficiency, defined as the cosine of the phase angle between and current. Unity power factor ($\cos\phi=1$) is

Detailed Problem: Thevenin Equivalent

Find the Thevenin equivalent circuit across terminals A and B for a circuit with a 10V source, 2Ω resistor, and 4Ω load.

Detailed Solution:

1. Remove load (4Ω). Find Open Circuit Voltage (V_{oc}).
2. $V_{th} = 10V * (R_2 / (R_1 + R_2))$ -- if using voltage divider.
3. For a simple series circuit, $V_{th} = 10V$.
4. Find R_{th} : Short circuit the voltage source. $R_{th} = 2\Omega$.
5. Final circuit: 10V source in series with 2Ω resistor connected to load.

5. Electrical Machines: DC & AC

Electromechanical Energy Conversion

DC Generator Works on Faraday's Law; converts mechanical energy to electrical energy using commutators to maintain DC output.

Induction Motor Works on the principle of a rotating magnetic field inducing a current in the rotor, resulting in torque.